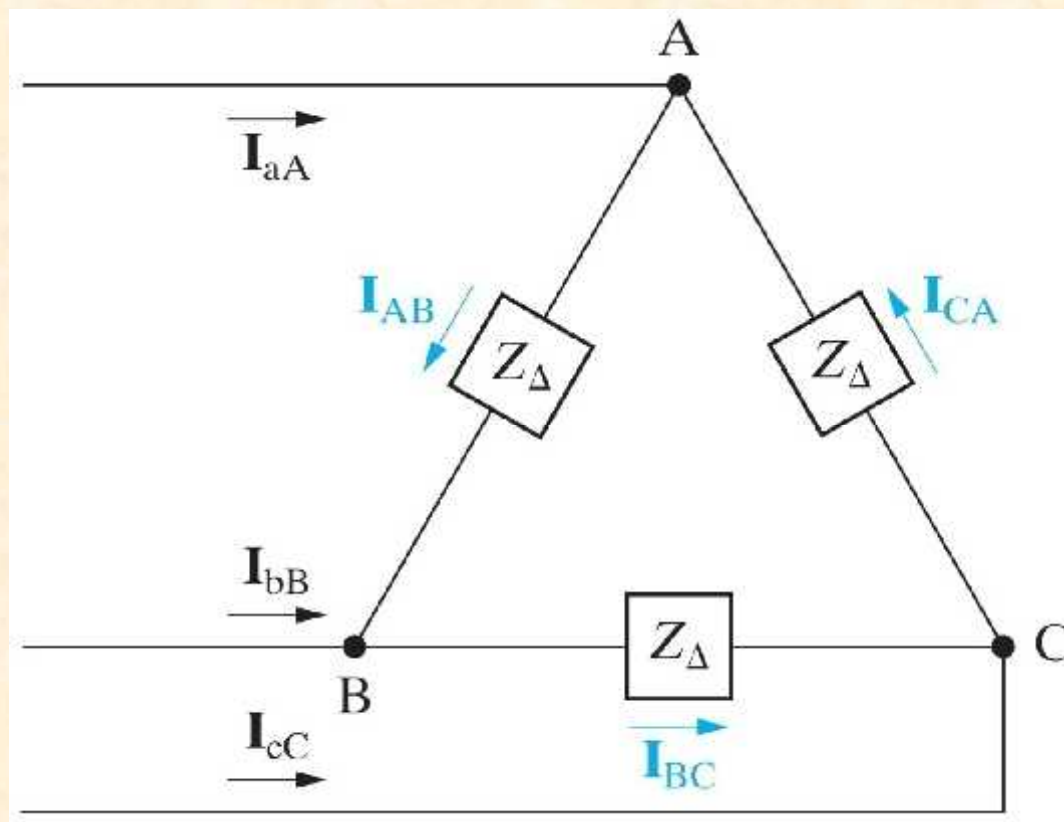


Balanced Δ -connected Load

✓ line voltages equal to phase voltages

$$V_L = V$$



Balanced Δ -connected Load

$$I_{AB} = \frac{V_{AB}}{Z}$$


$$I_{BC} = \frac{V_{BC}}{Z}$$

$$I_{CA} = \frac{V_{CA}}{Z}$$


$$I_{AB} = I_w \angle 0^\circ$$

$$I_{BC} = I_w \angle -120^\circ$$

$$I_{CA} = I_w \angle 120^\circ$$

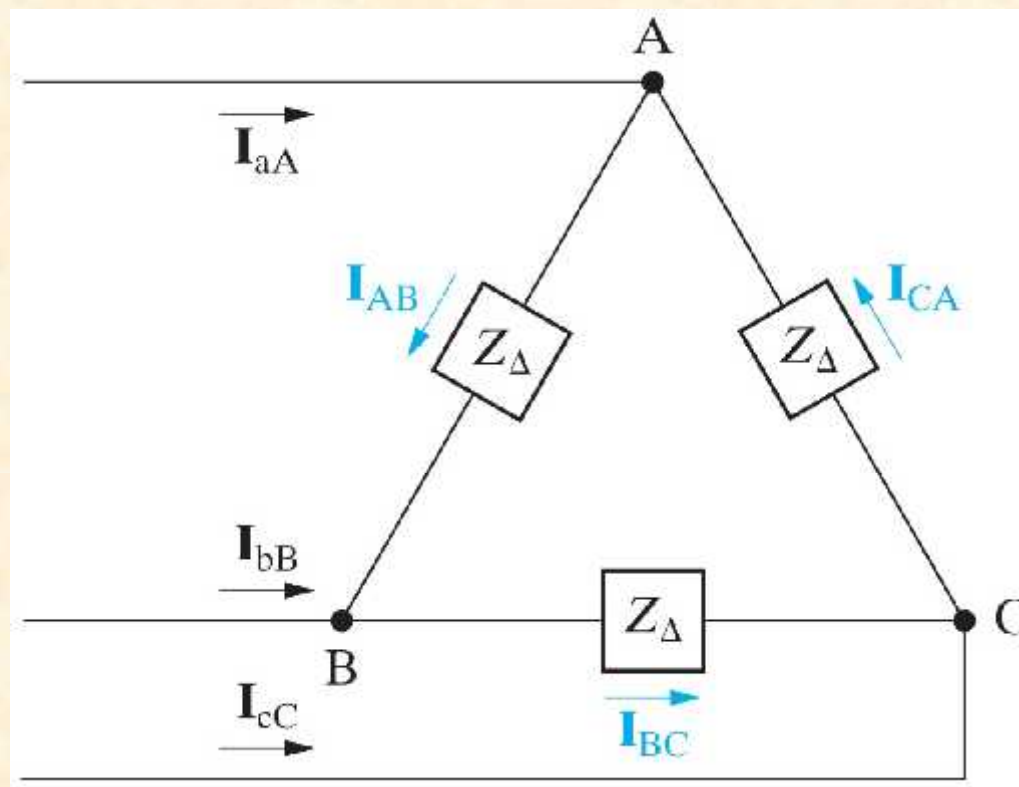

Balanced Δ -connected Load

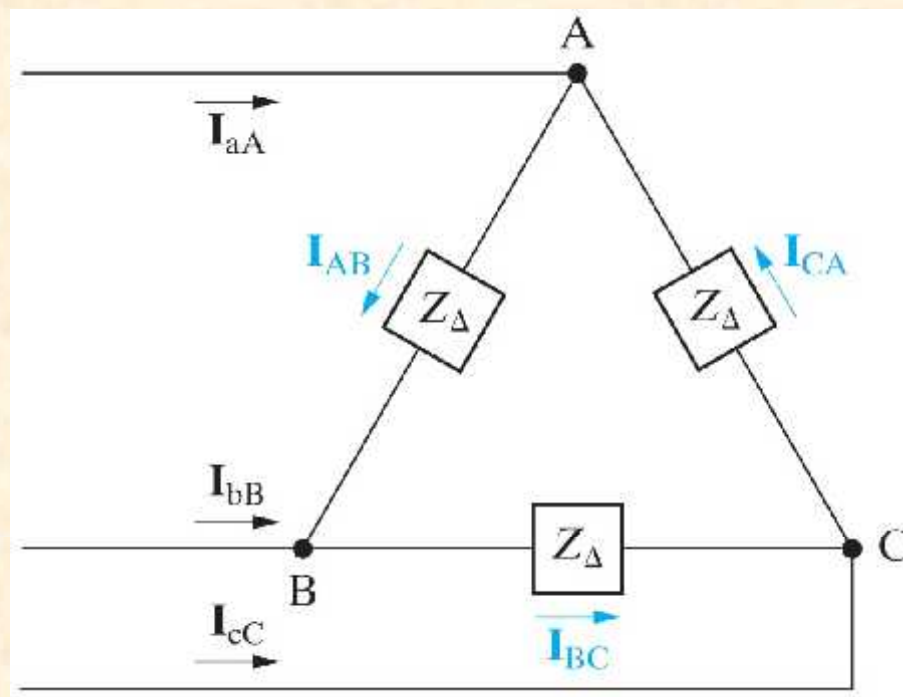

Line Currents

$$I_{aA} = I_{AB} - I_{CA}$$

$$I_{bB} = I_{BC} - I_{AB}$$


$$I_{cC} = I_{CA} - I_{BC}$$

Phase Currents




Line and Phase Currents for Balanced Δ -connected Load

for +ve
sequence

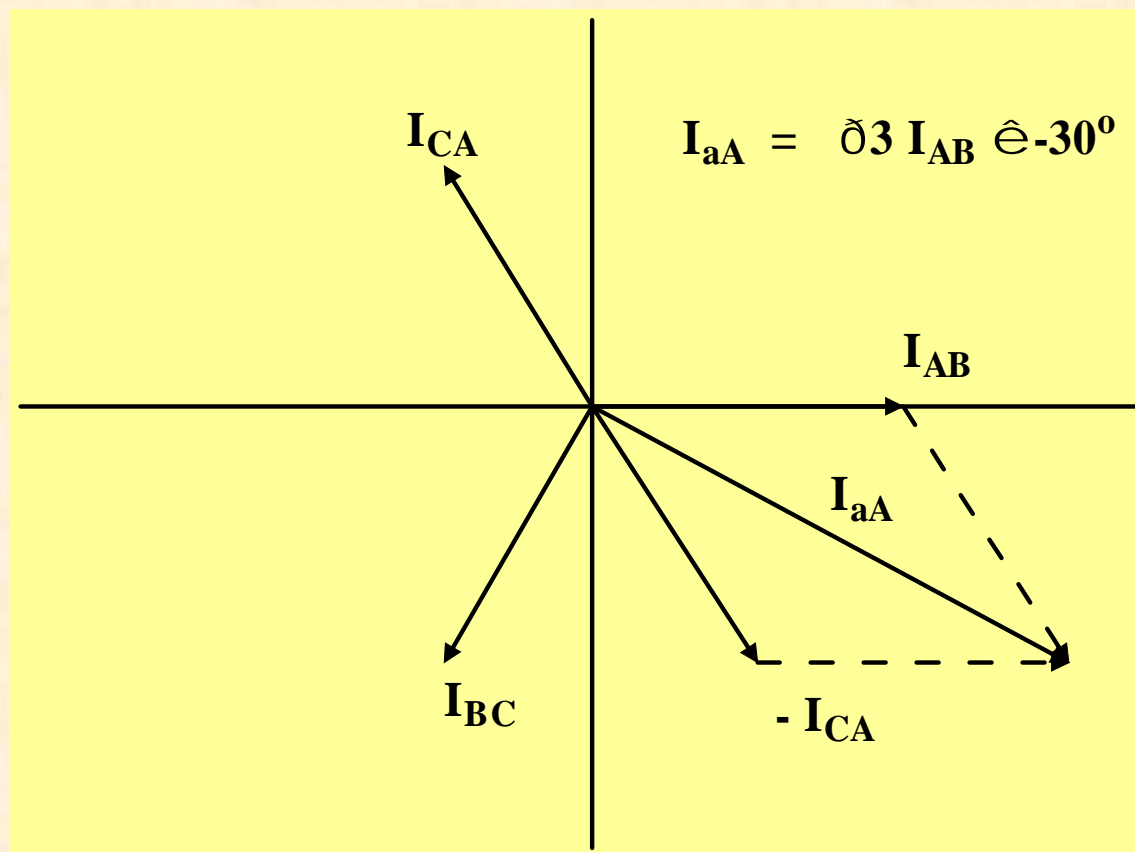

Line and Phase Currents for Balanced Δ -connected Load

for +ve
sequence

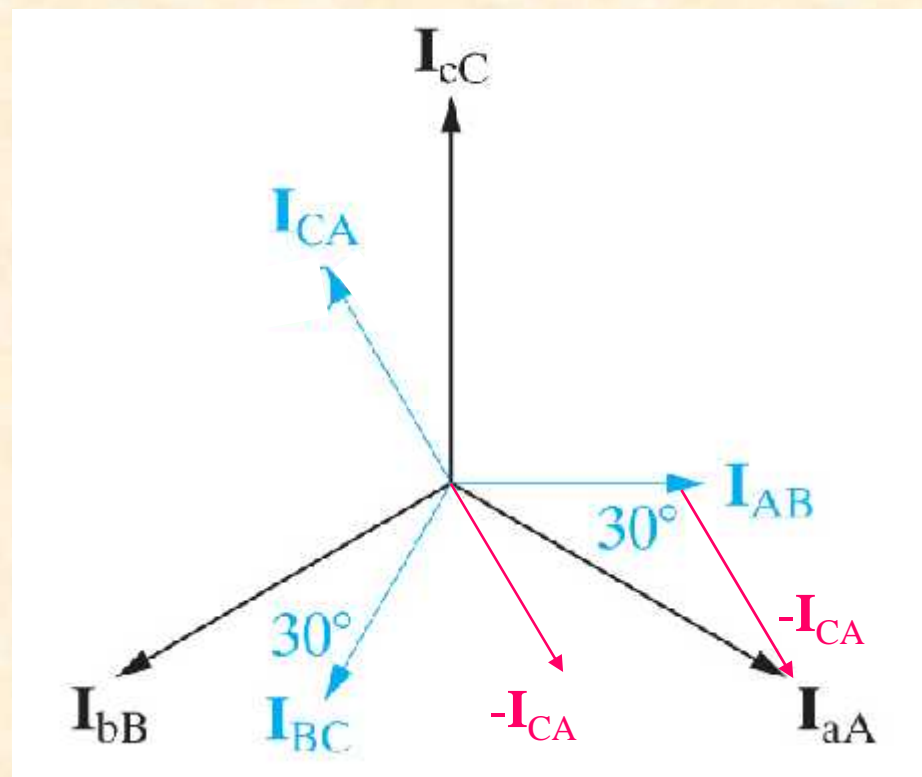

I_{aA} = Line Current

I = Phase Current

$$I_{aA} = \left(\sqrt{3} \angle -30^\circ \right) I$$



Line and Phase Currents for Balanced Δ -connected Load

PHASE CURRENTS (I_w)

$$I_{aA} = I_{AB} - I_{CA}$$

$$I_{bB} = I_{BC} - I_{AB}$$

$$I_{cC} = I_{CA} - I_{BC}$$



$$I_{aA} = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_{bB} = I_{aA} \angle -120^\circ$$

$$I_{cC} = I_{aA} \angle +120^\circ$$

LINE CURRENTS (I_L)

(for +ve sequence)



Conclusions for Balanced -connected Load

- The amplitude of the **line current** is equal to $\sqrt{3}$ times the phase current

$$|I_L| = \sqrt{3} |I_W|$$

- The set of line currents **lags** the phase currents by 30° (for +ve sequence)

$$\angle I_L = \angle I_W - 30^\circ$$


- The set of line currents **leads** the phase currents by 30° (for -ve sequence)

$$\angle I_L = \angle I_W + 30^\circ$$




Balanced Y- Three-Phase System

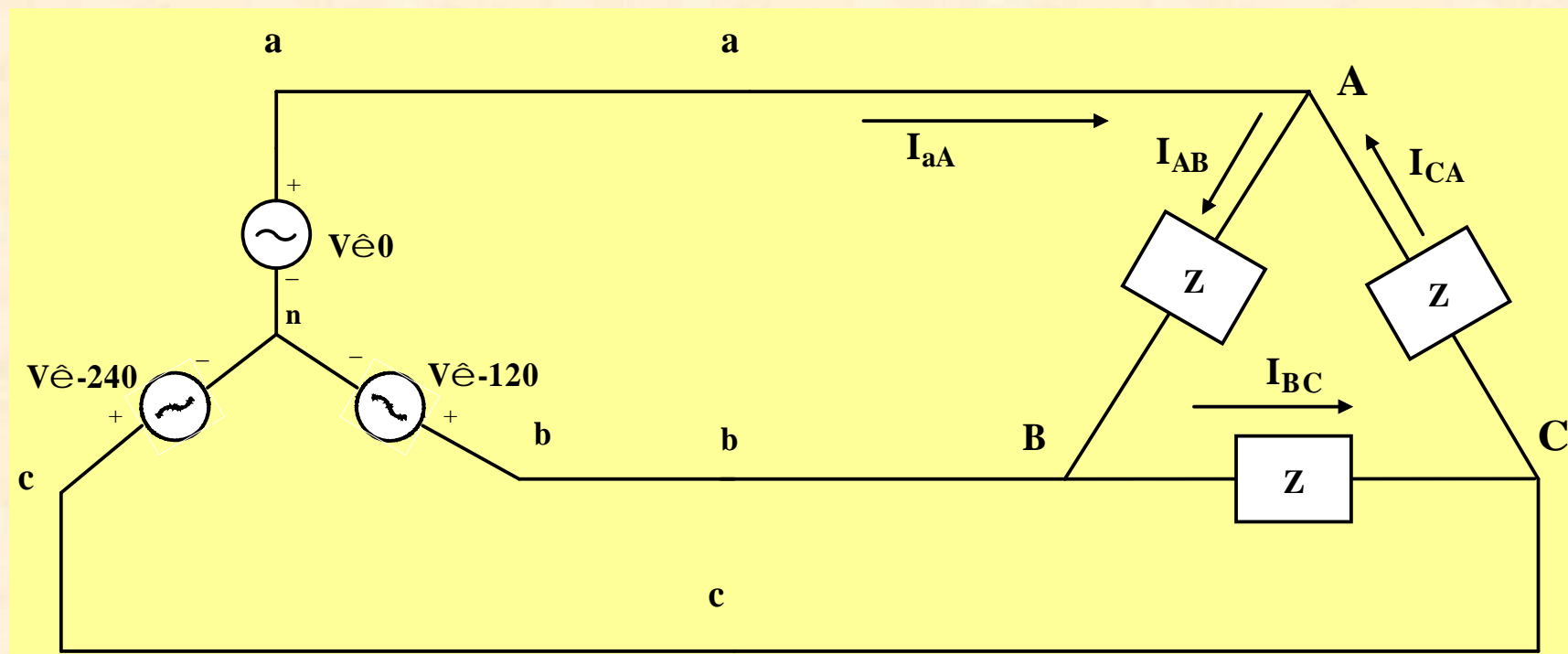- Three phase sources are usually Y-connected and three phase loads are Delta connected.
- There is **no neutral** connection for the Y- system




Balanced Y- Three-Phase System

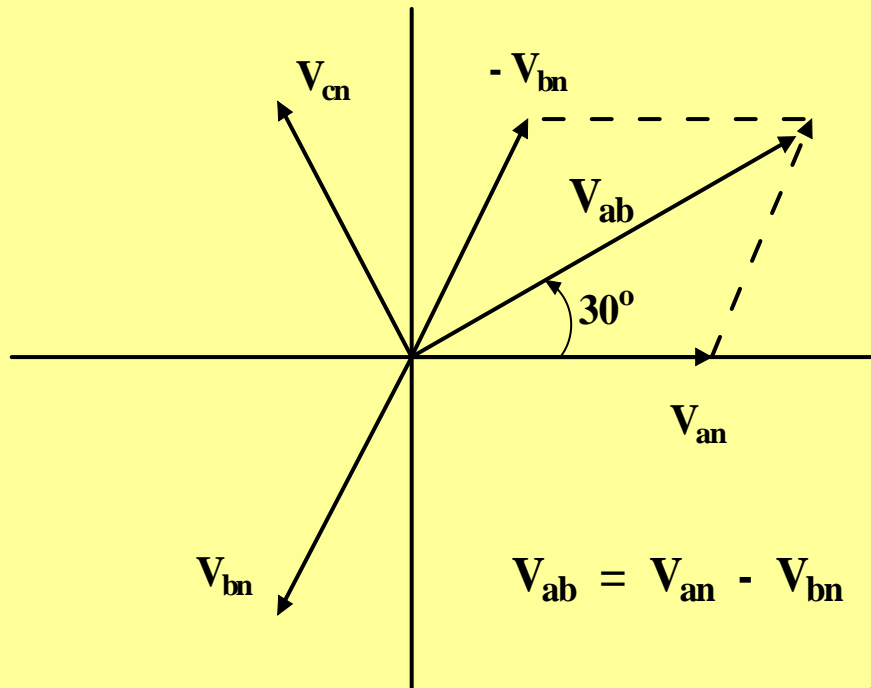

$$V_{ab} = V_{an} - V_{bn}$$
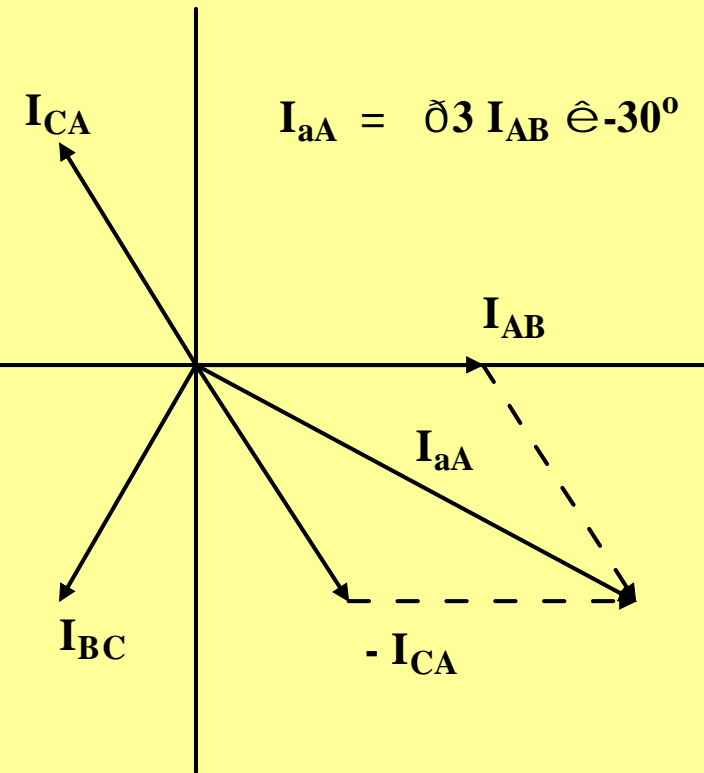
$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$




$$I_{aA} = \sqrt{3} I_{AB} \angle -30^\circ$$

for +ve
sequence



Balanced Y- Three-Phase System

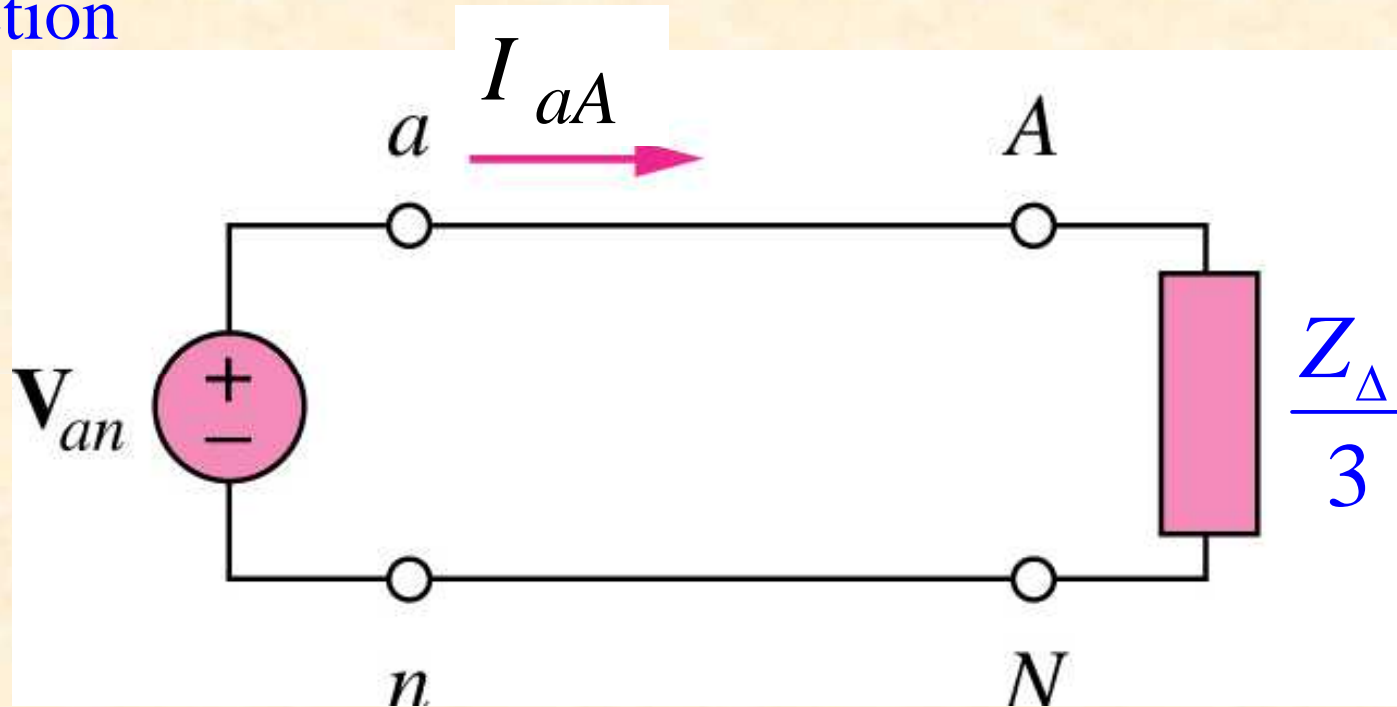➤ Single phase equivalent circuit of the balanced Y-connection



for +ve sequence $V_{AB} = \left(\sqrt{3} \angle 30^\circ \right) V_{AN}$ & $I_{AB} = I_{aA} / \left(\sqrt{3} \angle -30^\circ \right)$

for -ve sequence $V_{AB} = \left(\sqrt{3} \angle -30^\circ \right) V_{AN}$ & $I_{AB} = I_{aA} / \left(\sqrt{3} \angle 30^\circ \right)$



➤ Example on Y- System

The Y-connected source in Example 12.1 feeds a Δ -connected load through a distribution line having an impedance of $0.3 + j0.9 \Omega/\phi$. The load impedance is $118.5 + j85.8 \Omega/\phi$. Use the a-phase internal voltage of the generator as the reference.

- Construct a single-phase equivalent circuit of the three-phase system.
- Calculate the line currents \mathbf{I}_{aA} , \mathbf{I}_{bB} , and \mathbf{I}_{cC} .
- Calculate the phase voltages at the load terminals.
- Calculate the phase currents of the load.
- Calculate the line voltages at the source terminals.



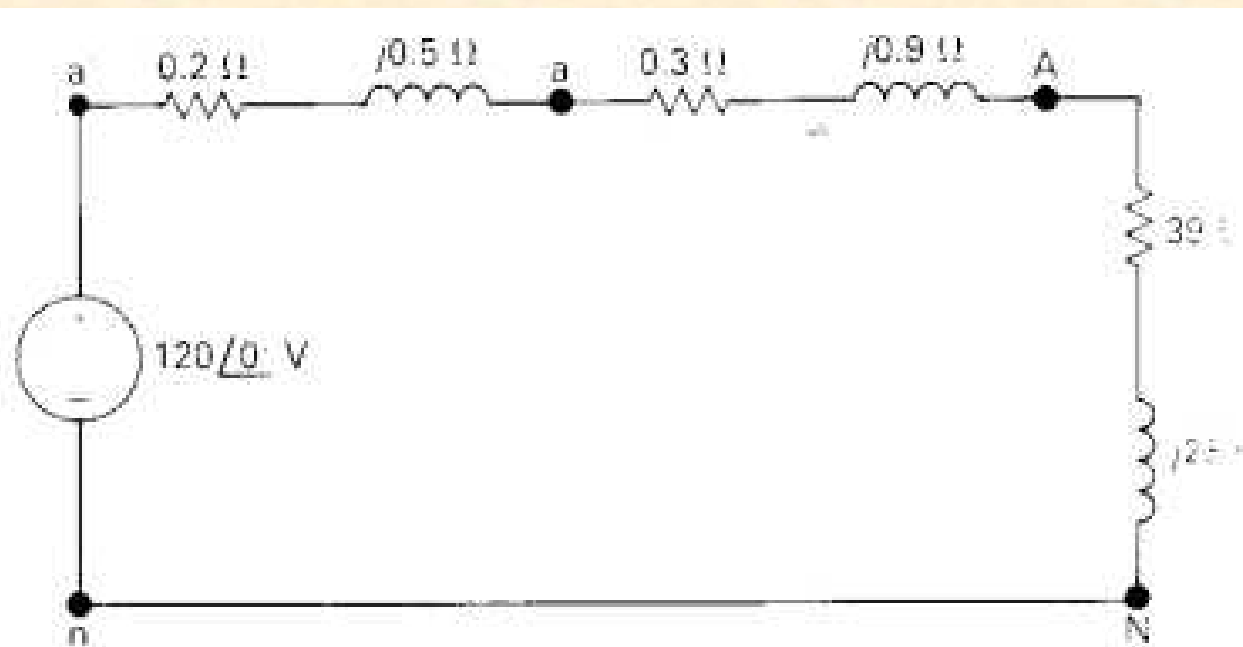


FIGURE 12.13 The single-phase equivalent circuit for Example 12.2.

- a) Figure 12.13 shows the single-phase equivalent circuit. The load impedance of the Y-equivalent is

$$\left(\frac{1}{3}\right)(118.5 + j85.8) \quad \text{or} \quad 39.5 + j28.6 \, \Omega/\phi.$$



b) The a-phase line current is

$$\begin{aligned}\mathbf{I}_{aA} &= \frac{120/0^\circ}{(0.2 + 0.3 + 39.5) + j(0.5 + 0.9 + 28.6)} \\ &= \frac{120/0^\circ}{40 + j30} = 2.4/\underline{-36.87^\circ} \text{ A.}\end{aligned}$$

Hence

$$\mathbf{I}_{bB} = 2.4/\underline{-156.87^\circ} \text{ A;}$$

$$\mathbf{I}_{cC} = 2.4/\underline{83.13^\circ} \text{ A.}$$



c) As the load is Δ -connected, the phase voltages are the same as the line voltages. To calculate the line voltages, we first calculate V_{AN} :

$$\begin{aligned} V_{AN} &= (39.5 + j28.6)(2.4 \angle -36.87^\circ) \\ &= 117.04 \angle -0.96^\circ \text{ V.} \end{aligned}$$

Because the phase sequence is positive, the line voltage V_{AB} is

$$\begin{aligned} V_{AB} &= \sqrt{3} \angle 30^\circ V_{AN} \\ &= 202.72 \angle 29.04^\circ \text{ V.} \end{aligned}$$

Therefore

$$\begin{aligned} V_{BC} &= 202.72 \angle -90.96^\circ \text{ V;} \\ V_{CA} &= 202.72 \angle 149.04^\circ \text{ V.} \end{aligned}$$



d) The phase currents of the load may be calculated directly from the line currents:

$$\begin{aligned} \mathbf{I}_{AB} &= \frac{1}{\sqrt{3}} \angle 30^\circ \mathbf{I}_{aA} \\ &= 1.39 \angle -6.87^\circ \text{ A.} \end{aligned}$$

Once we know \mathbf{I}_{AB} , we also know the other load phase currents:

$$\begin{aligned} \mathbf{I}_{BC} &= 1.39 \angle -126.87^\circ \text{ A;} \\ \mathbf{I}_{CA} &= 1.39 \angle 113.13^\circ \text{ A.} \end{aligned}$$

Note that we can check the calculation of \mathbf{I}_{AB} by using the previously calculated \mathbf{V}_{AB} and the impedance of the Δ -connected load. That is,

$$\begin{aligned} \mathbf{I}_{AB} &= \frac{\mathbf{V}_{AB}}{Z_\phi} = \frac{202.72 \angle 29.04^\circ}{118.5 + j85.8} \\ &= 1.39 \angle -6.87^\circ \text{ A.} \end{aligned}$$

(Alternative methods of calculation help eliminate errors, and we highly recommend their use in all work involving analysis and design.)



c) To calculate the line voltage at the terminals of the source, we first calculate V_{an} . Figure 12.13 shows that V_{an} is the voltage drop across the line impedance plus the load impedance, so

$$\begin{aligned} V_{an} &= (39.8 + j29.5)2.4 \angle -36.87^\circ \\ &= 118.90 \angle -0.32^\circ \text{ V.} \end{aligned}$$

The line voltage V_{ab} is

$$V_{ab} = \sqrt{3} \angle 30^\circ V_{an} \quad \text{or} \quad V_{ab} = 205.94 \angle 29.68^\circ \text{ V.}$$

Therefore

$$V_{bc} = 205.94 \angle -90.32^\circ \text{ V;}$$

$$V_{ca} = 205.94 \angle +149.68^\circ \text{ V.}$$



Common Source-Load Connection

- ✓ Common connection of source: **Y**
 - -connected sources: the circulating current may result in the delta mesh if the three phase voltages are slightly unbalanced.
- ✓ Common connection of load:
 - Y-connected load: neutral line may not be accessible, load can not be added or removed easily.

